


AC Bridges

❑ Supply – Alternating Current Source
Detector –

Normal Commercial Frequency -
Vibration Galvanometer
High Frequency - Headphone

Two Types of AC Bridge –
Ratio Bridge
Product Bridge

Wheatstone bridge

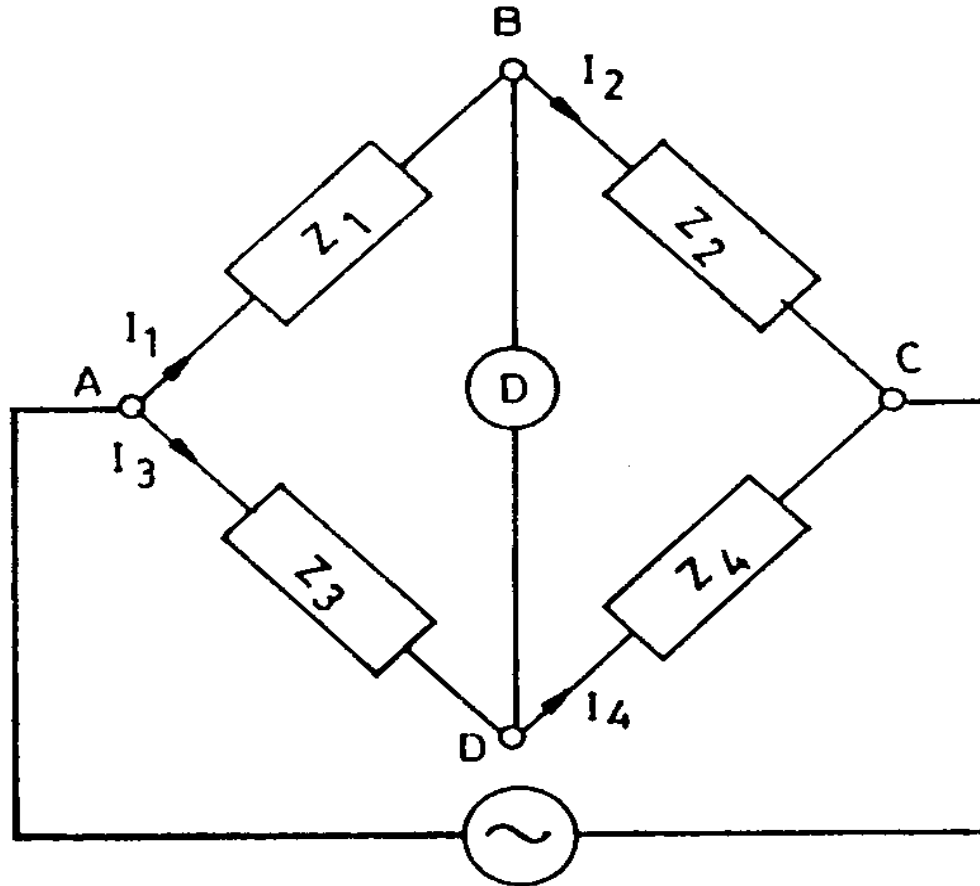

General Four Arm AC Bridge

Ratio Bridge:-

- $Z_1 Z_4 = Z_2 Z_3$

$$Z_1 = \frac{Z_2 Z_3}{Z_4}$$

- Consider the ratio arms Z_2, Z_4 or Z_3, Z_4

- i.e. $\frac{Z_2}{Z_4} = (A \pm jB)$

- Again $Z_1 = Z_3(A \pm jB)$
- $(R_1 \pm jX_1) = (R_3 \pm jX_3)(A \pm jB)$

- **When the ratio arms are real**

- $R_1 = AR_3$ or $R_1 = AR_2$
- $X_1 = AX_3$ or $X_1 = AX_2$

- **When the ratio arms are imaginary**

- $R_1 = -BX_3$ or $R_1 = -BX_2$
- $X_1 = BR_3$ or $X_1 = BR_2$

Product Bridge:-

- $Z_1 Z_4 = Z_2 Z_3$

$$Z_1 = \frac{Z_2 Z_3}{Z_4}$$

- Consider the product arm Z_2, Z_3 in form of $(A \pm jB)$

$$(R_1 \pm jX_1) = \frac{A \pm jB}{Z_4} = (A \pm jB)Y_4 = (A \pm jB)(G_4 \pm jB_4)$$

- Admittance $Y_4 = \left(\frac{1}{R_4} \pm \frac{1}{jX_4} \right) = (G_4 \pm jB_4)$
= (Conductance $\pm j$ Susceptance)

- **For product arms real**

- $R_1 = AG_4$
- $X_1 = AB_4$

- **For product arms imaginary**

- $R_1 = -BB_4$
- $X_1 = BG_4$

- For Product Bridge Standard arm must be connected in parallel.

❖ **Measurement of Inductance**

- Maxwell's Bridge
- Maxwell-Wein Bridge
- Anderson Bridge
- Hey Bridge
- Owen Bridge

❖ **Measurement of Capacitance**


- De Sauty's Bridge
- Schering Bridge
- High Voltage Schering Bridge

❖ **Measurement of Frequency**

- Wein's Bridge

Maxwell's Bridge:

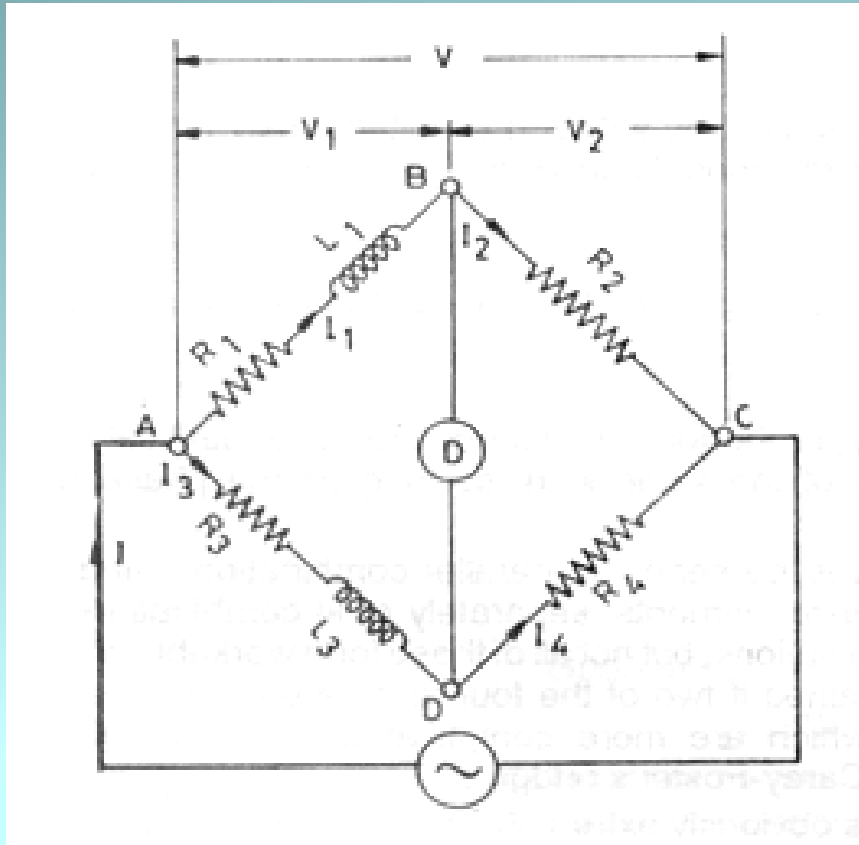Accurate measurement of medium inductance




$$R_1 = \frac{R_2}{R_4} R_3$$

$$L_1 = \frac{R_2}{R_4} L_3$$

Maxwell-Wein Bridge:

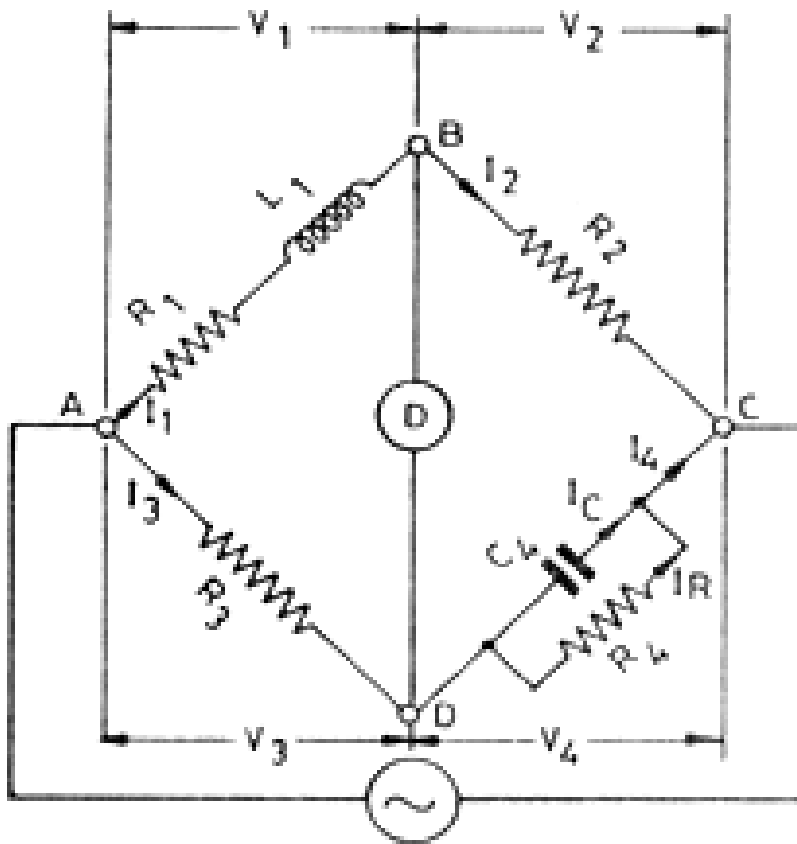Measurement of self inductance with a standard variable capacitance




$$R_1 = \frac{R_2 R_3}{R_4}$$

$$L_1 = R_2 R_3 C_4$$

$$Q = \frac{\omega L_1}{R_1} = \omega C_4 R_4$$

Anderson Bridge:

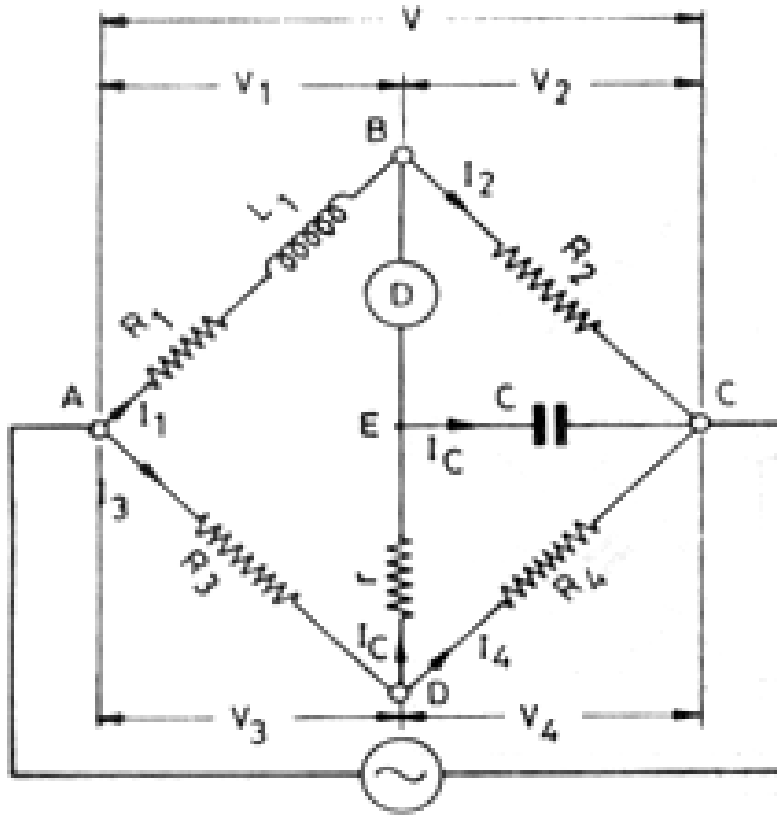Measurement of Self inductance in terms of known capacitance and resistance over a wide range




$$R_1 = \frac{R_2}{R_4} R_3$$

$$L_1 = \frac{CR_2}{R_4} [r(R_3 + R_4) + R_3R_4]$$

Hey Bridge

Modified Maxwell-Wein Bridge

Measured inductor's phase angle large

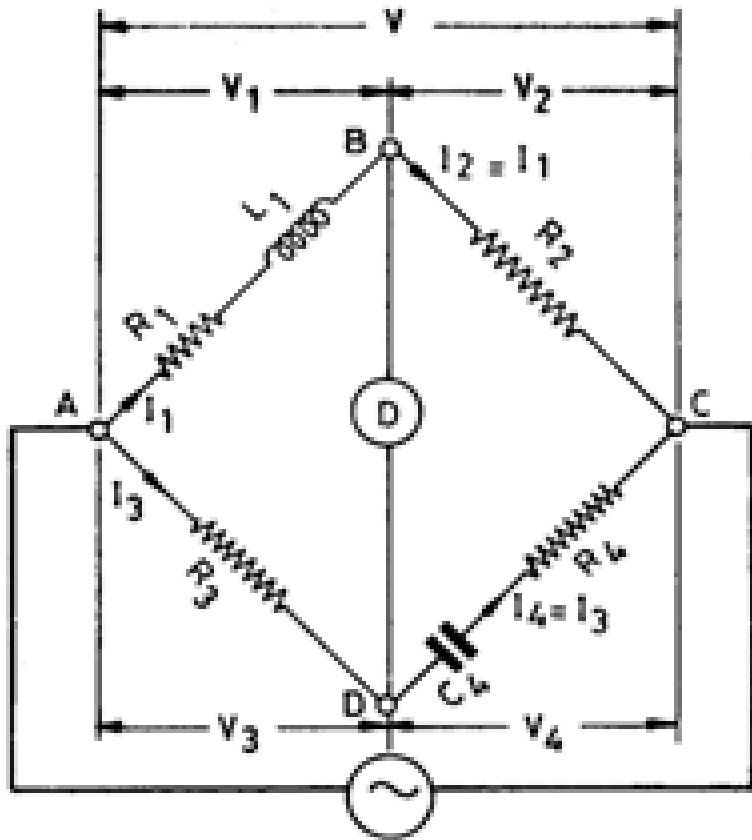


$$R_1 = \frac{R_2 R_3 R_4 C_4^2 \omega^2}{1 + \omega^2 C_4^2 R_4^2}$$

$$L_1 = \frac{R_2 R_3 C_4}{1 + \omega^2 C_4^2 R_4^2}$$

$$Q = \frac{1}{\omega R_4 C_4}$$

Owen Bridge:

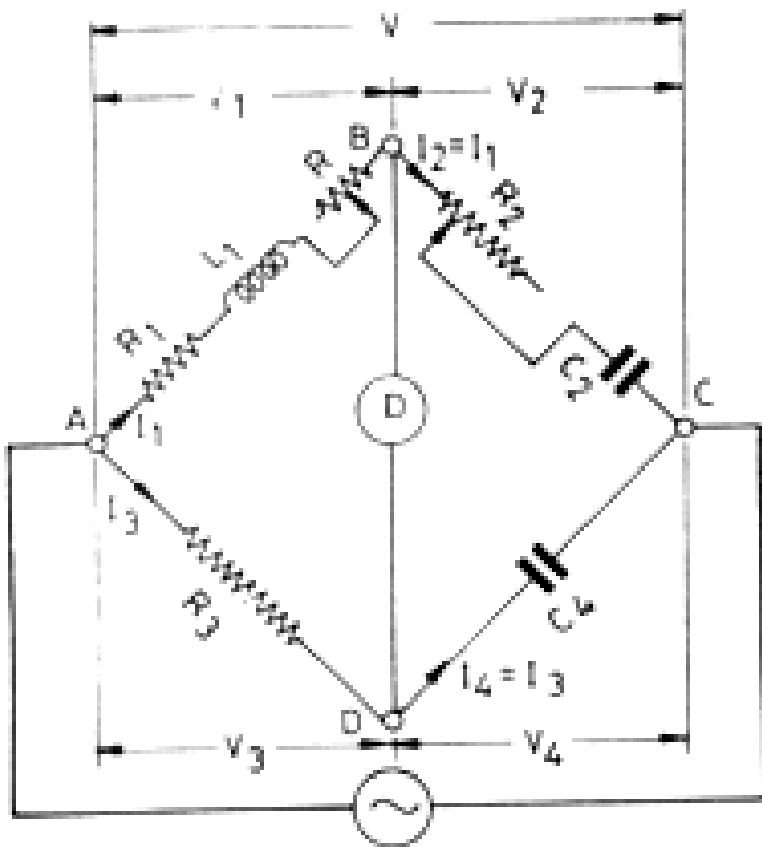Measurement of inductance in a wide range




$$R_1 = \frac{R_3 C_4}{C_2} - R$$

$$L_1 = R_2 R_3 C_4$$

De Sauty's Bridge:

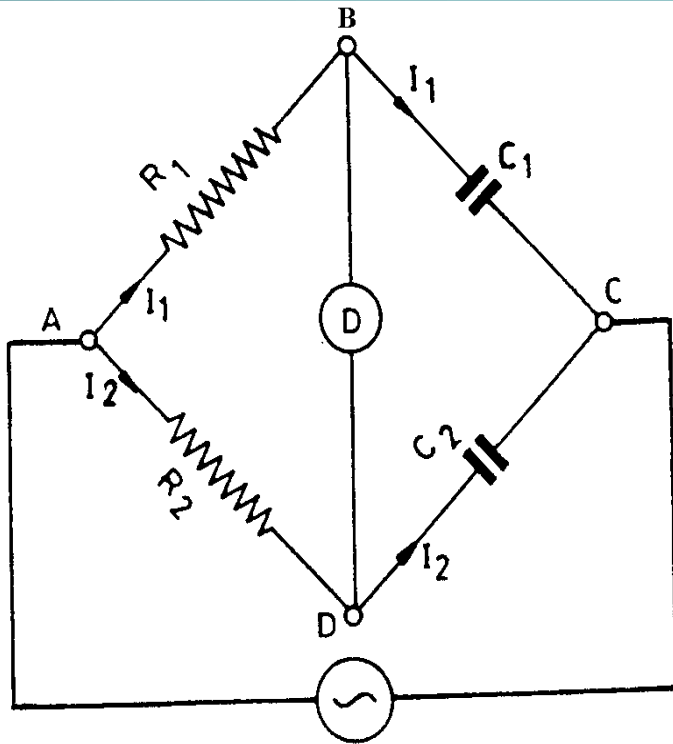
Measurement of Capacitance with respect of known standard capacitance



$$C_1 = C_2 \frac{R_2}{R_1}$$

Schering Bridge:

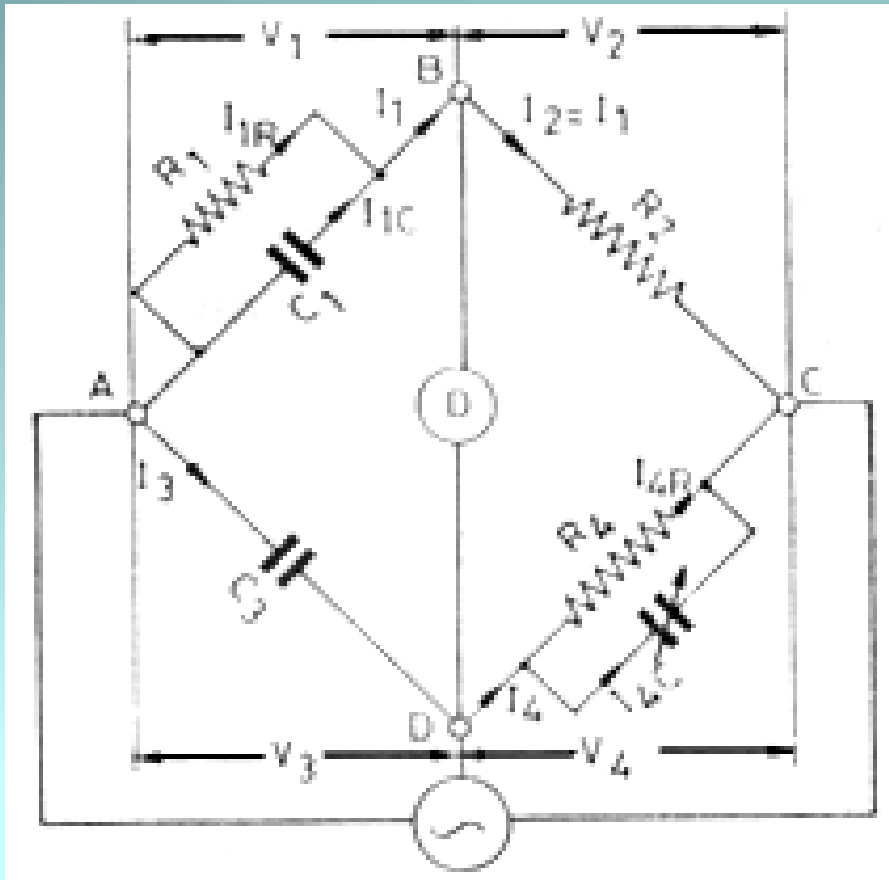Measurement of capacitance with respect of a variable capacitance




$$R_1 = \frac{1}{\omega^2 C_1 C_4 R_4}$$

$$C_1 = \frac{C_3 R_4 \cos^2 \delta}{R_2}$$

$$\delta = \tan^{-1} \left(\frac{1}{\omega C_1 R_1} \right)$$


High Voltage Schering Bridge:

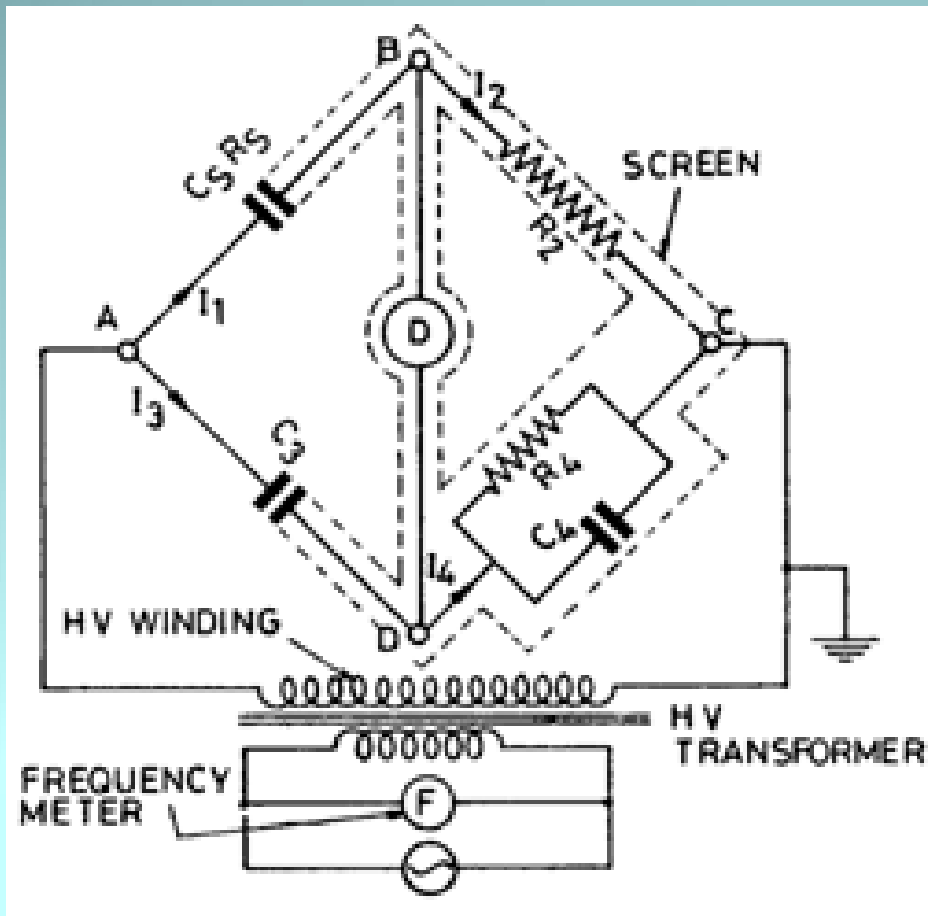Measurement of capacitance, dielectric loss of a capacitance and power factor of cables



Wien's Bridge:

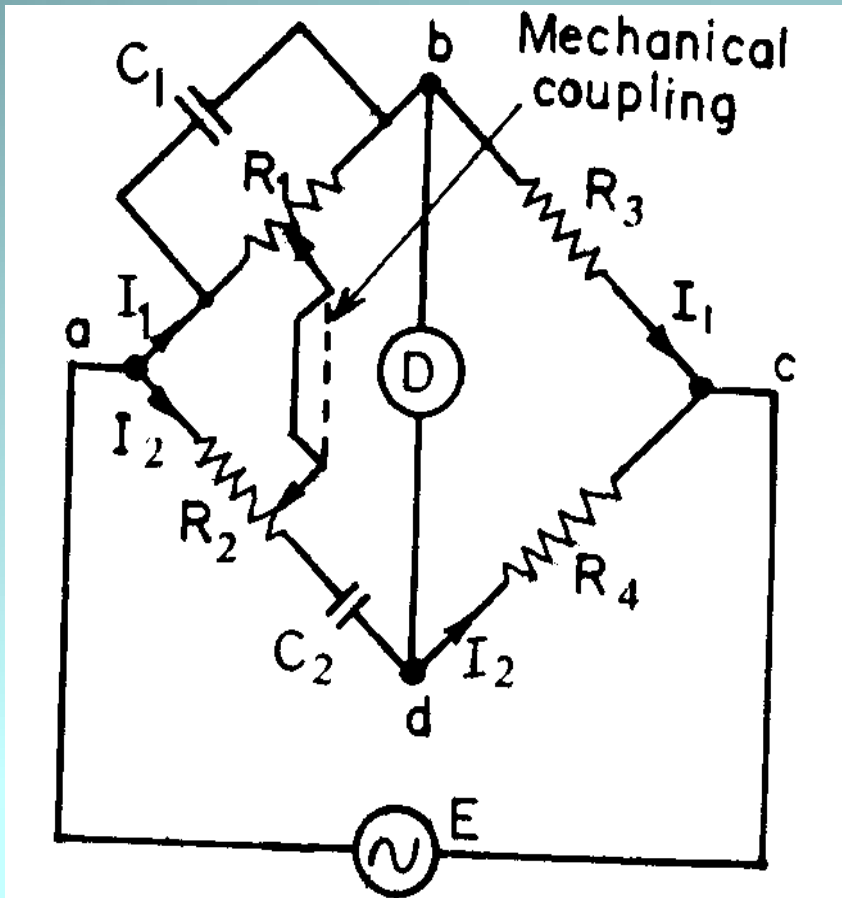Used for audio and HF oscillators as a frequency determining device



$$f = \frac{1}{2\pi\sqrt{R_1R_2C_1C_2}}$$